

R&D on Counting Pixel Chips


Yunpeng Lu

Outline

- Motivation
- Fundamental Issues
- Current Mirror & Amp-Sha-Disc
- Nested-Wells & DSOI
- Summary

Motivation(1)

- Shielding is a key issue in SOI Pixel Technology, and Counting Pixel is an effective measure to study it.
 - Necessity of shielding was recognized and understood by F. X. Pengg
 - Integrating pixel works fine with BPW suppressing back gate effect (Why no charge injection observed? Slow slew rate/ Cancelled by integration?)
 - But in counting pixel, charge injection messed up the counting results.

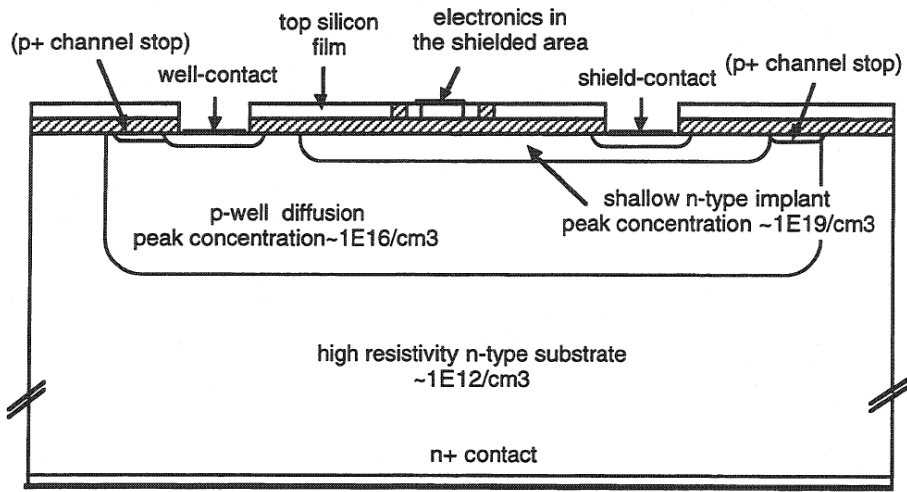

Shielding-well proposed by F. X. Pengg in his dissertation “Monolithic Silicon Pixel Detectors in SOI Technology”

Good concept but not implemented successfully.


Figure(2.11a): The n⁺-p-n⁻ structure of shield and well in the high resistivity substrate, cut.

Motivation(2)


- Counting Pixel is getting more and more popular in synchrotron radiation application.
- Particularly interested in the area detector proposed by Prof. Kishimoto.
 - 30 μm^2 pixel size
 - 1k frames/s
 - 14 bit counter
 - Low energy X-ray 2~4 keV

Very compact pixel circuit
and good S/N required!

Ferroelectricity in a molecular crystal

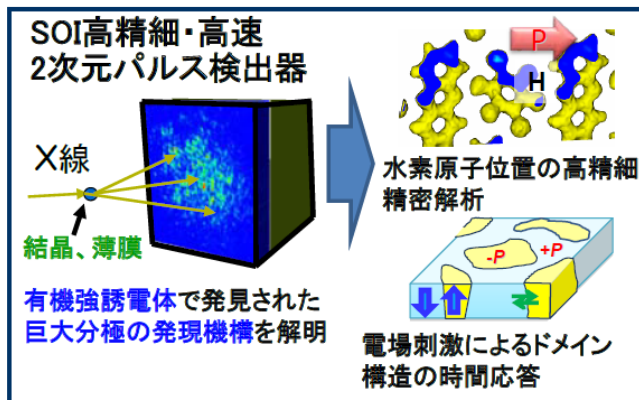

Structure change of a cell membrane

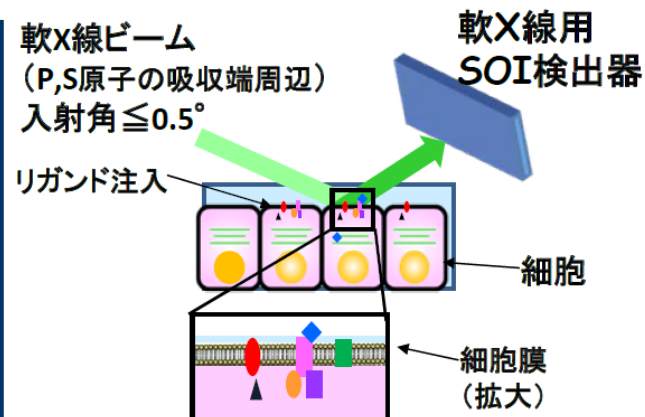

Fundamental Issues

- On-chip circuit
 - Amp-Sha-Disc system
 - Counter and register in pixel
- Shielding
 - Nested-wells
 - Double SOI
- Leakage current
 - Low temperature would mitigate it
- Radiation damage
 - Should be fine if back-illuminated by low energy X-ray

Review of CPIXTEG2 results

- ✓ Amp-Sha-Disc system
- ✓ Counter and Register
- ✓ Bias and Aobuf
- Current Source variation
- ✓ Shielding between analog and sense node
- ✓ Response of Light stimulus
- Shielding between counter and sense node not reported

A-R-Tec Confidential
2012/3/19 大本・今村

測定実施TEG一覧


N基板用及び[N,P]基板共用TEG

TEG種別	TEG番号	チップID番号					コメント
		1	2	3	4	5	
pixel array	PA-1C N	○					レジスタ(CSR,DATA)読み書き確認のみ
	PA-2C N	○					レジスタ(CSR,DATA)読み書き確認のみ
cross-talk	0-1C N	○					
	0-2C N	○					
	0-3C N	○					
	0-4C N	○					
preamp+ shaper+ discri	1-1C N	○					
	1-2C N	○					
	1-3C N	○					
	1-4C N	○					
	1-5C N	○					
preamp+ shaper	2-1C N	○	○				
	2-2C N	○	○				
	2-3C N	○	○				
	2-4C N	○	○				
	2-5C N	○	○				
preamp	3-1C N	○	○	○			
	3-2C N	○	○	○			
	3-3C N	○	○	○			
shaper	4-1C	○					TEGアレイ中のshaper(TEG1X,2X)の測定でshaperの特性を評価
	4-4C	○					
discri	5-1C N	○	○	○			
aobuf		○	○	○	○	○	
bias		○	○	○	○	○	

P基板用TEG

TEG種別	TEG番号	チップID番号					コメント
		1	2	3	4	5	
pixel array	PA-1C P	○					レジスタ(CSR,DATA)読み書き確認のみ
	PA-2C P	○					レジスタ(CSR,DATA)読み書き確認のみ
cross-talk							
preamp+ shaper+ discri	1-1C P						
	1-2C P						
	1-3C P						
	1-4C P						
	1-5C P						
preamp+ shaper	2-1C P						
	2-2C P						
	2-3C P						
	2-4C P						
	2-5C P						
preamp	3-1C P						
	3-2C P						
	3-3C P						
shaper							
discri	5-1C P	○	○	○			
aobuf							
bias							


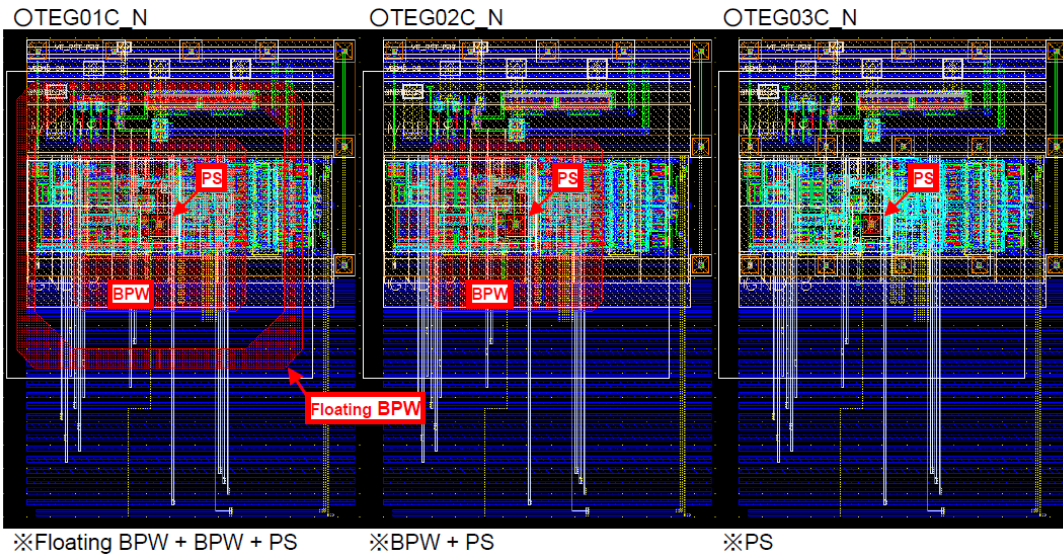
Continuing efforts of Nested-wells on CPIXTEG3



New nested-wells layout:

- Expand to full pixel
- More BNW contacts



CPIXTEG3
TEG04C_N

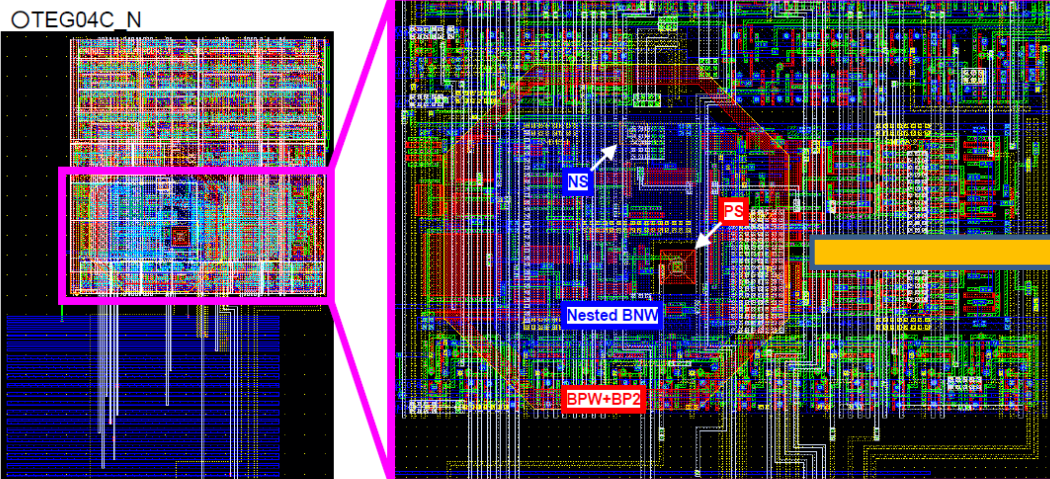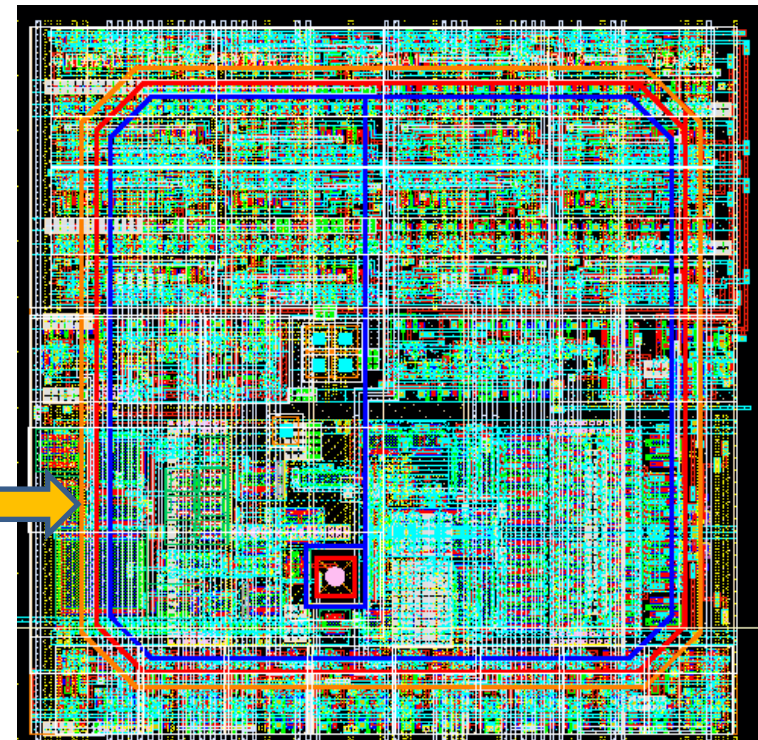

※BPW + Nested BNW


Findings though CPIXTEG2/3

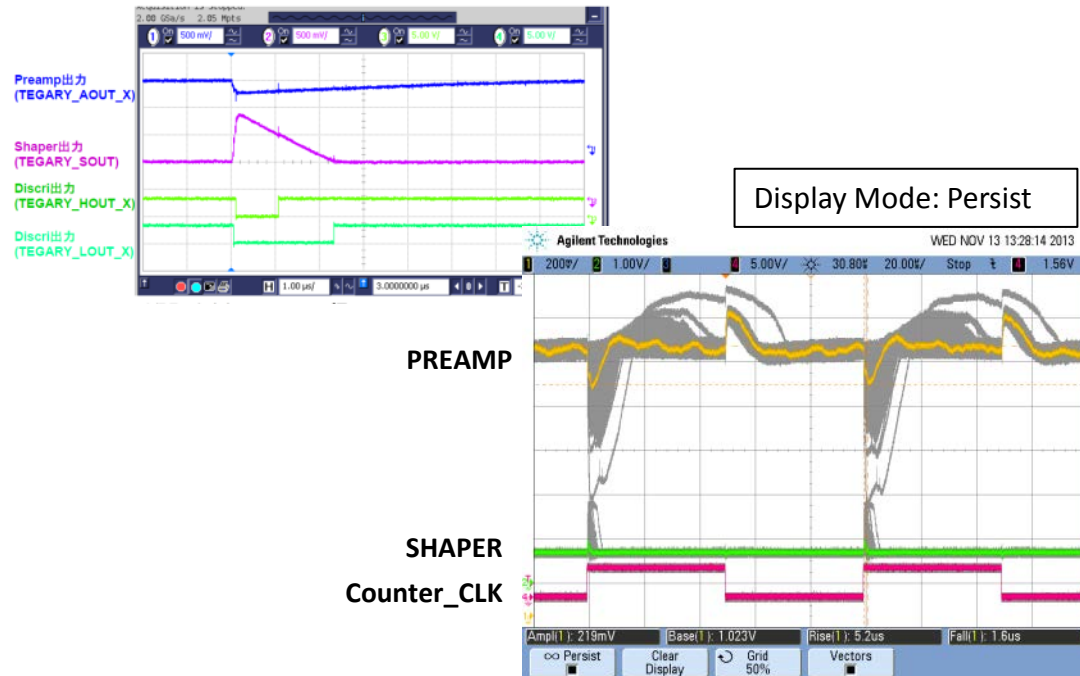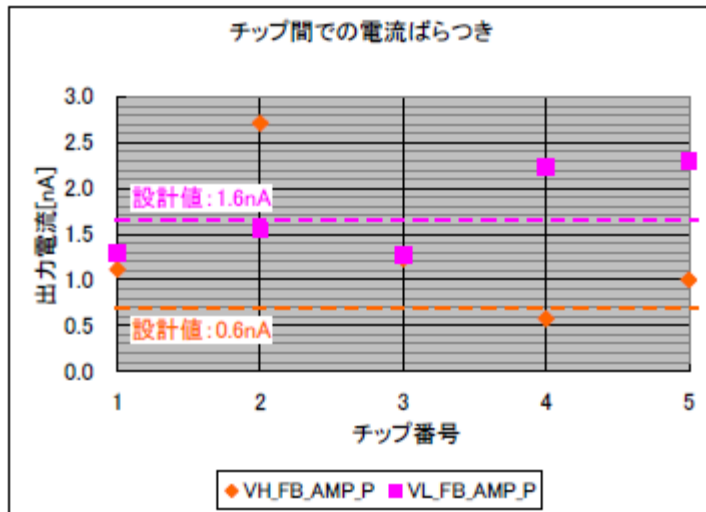- Low current source variation (double checked)
- Insufficient shielding efficiency if the sense node overlaps with Discriminator or Counter (measured on CPIXTEG3)
 - Shielding between shaper and sense node is good (double checked)
- A new chip CPIXTEG3b designed on basis of above findings.




The Krummenacher Scheme and current source

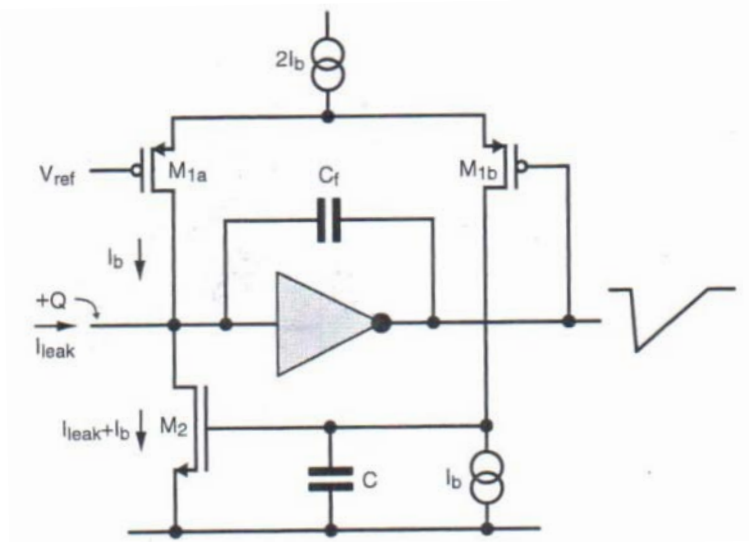
- The kummenacher scheme was adopted for Preamp and Shaper in cpixteg2/3 design.
 - Baseline of output can be set by V_{ref} , which is good for DC coupling to the next discrimination stage.
 - However, its operation relies on the exact ratio of I_{source_h} and I_{source_l} .



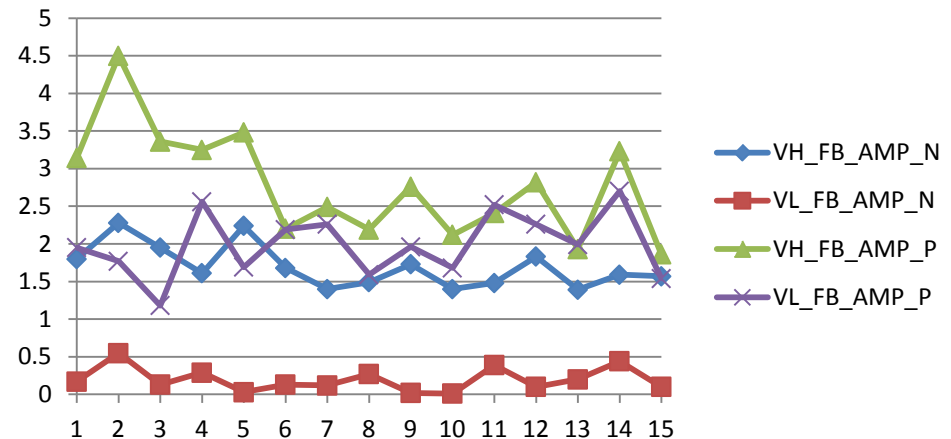- CPIXTEG3 Measurement
- PMOS current increased dramatically!
 - $VH_FB_AMP_N/VL_FB_AMP_N=1.0nA/0.55nA$ (SPICE)
 - $VH_FB_AMP_P/VL_FB_AMP_P=0.53nA/1.1nA$ (SPICE)



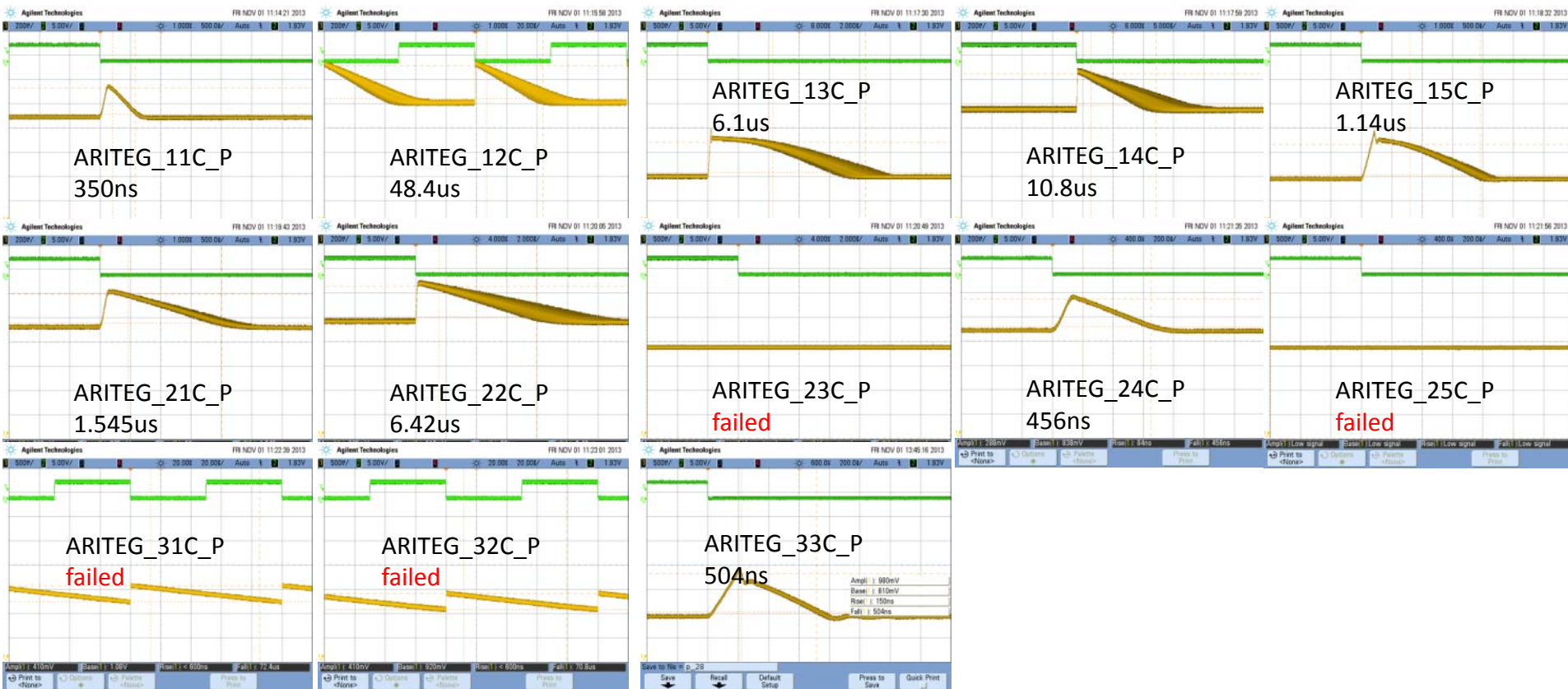
- PREAMP is not supposed to work with $VH_FB_AMP_P/VL_FB_AMP_P=3.14nA/1.95nA$ (0.53nA/1.1nA by SPICE).
 - Feedback current $\sim (VL_FB_AMP_P - VH_FB_AMP_P)$
- Some PREAMPs among the 13 TEG elements did fail to operate.
 - Others showed quite different falling edge, which implies different feedback current



350ns falling edge $\sim 4.6nA$ feedback current
 48.4us falling edge $\sim 0.033nA$ feedback current
 6.1us falling edge $\sim 0.26nA$ feedback current





Constant Current Feedback

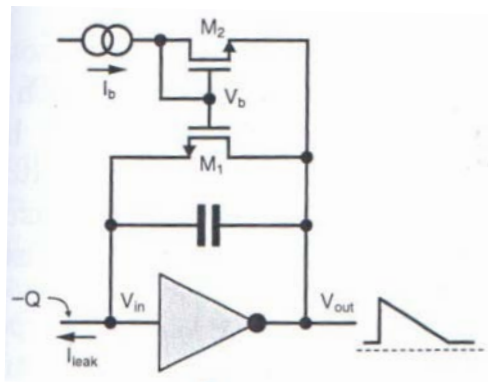- Constant current feedback structure is less dependent on the precision of low current source.
 - Variation of current source only changes falling edge but the amplifier would still operate.
 - V_{out} depends on the V_{th} of input transistor, leakage current and DC operating point of feedback transistor.
 - DC coupling to discriminator is not a good choice any more.





Differential-pair discriminator

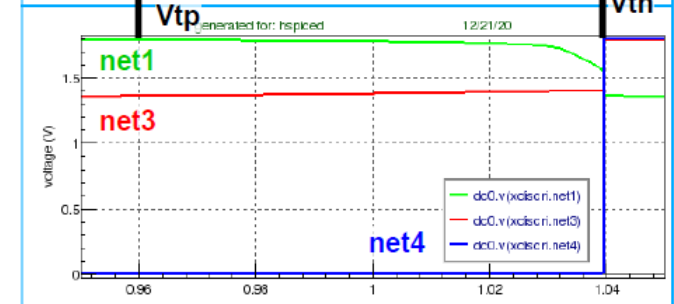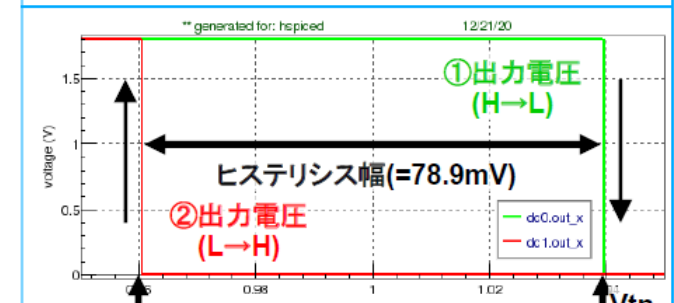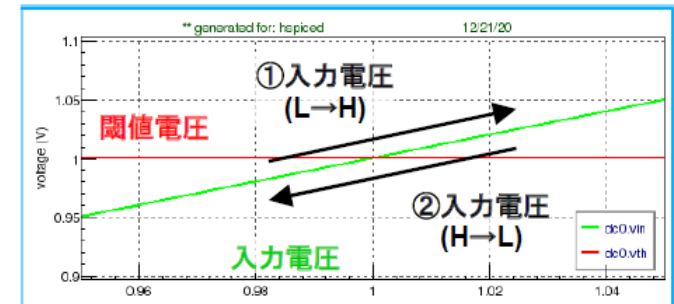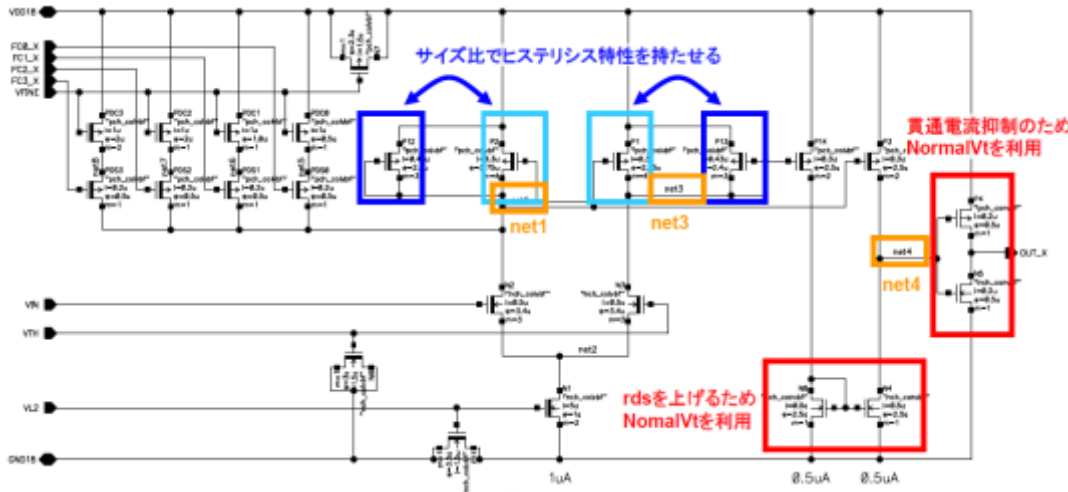- DC coupled discriminator used in CPIXTEG2/3.
 - Differential pair with composite load(a diode-connected transistor and another one operated in linear region)
 - Hysteresis
 - DAC coded current to adjust the local threshold




Diode-biased-inverter discriminator

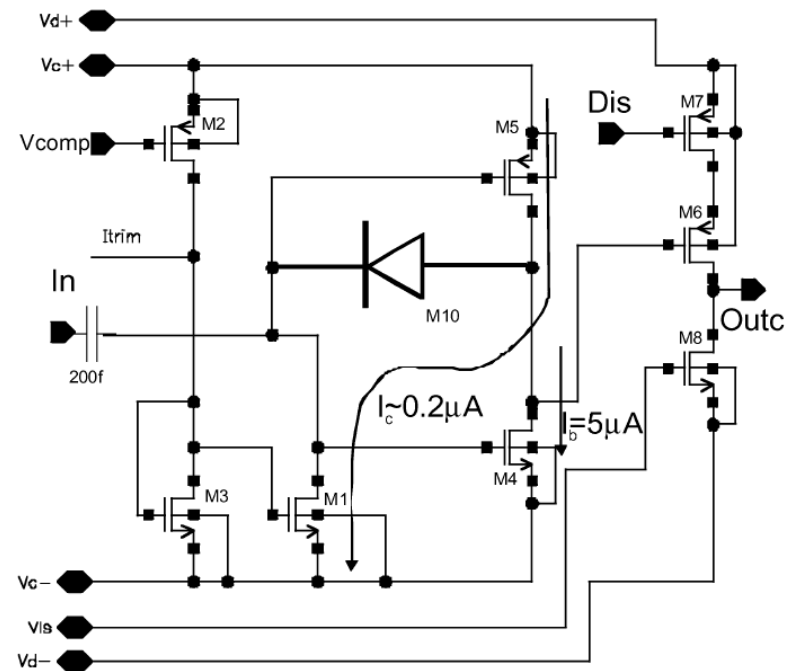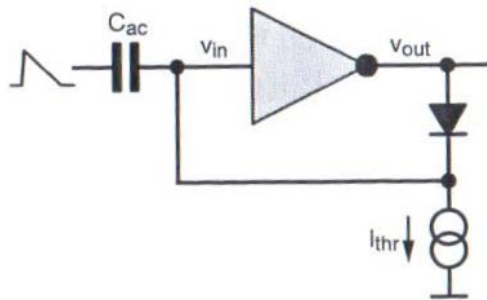- Used in the PILATUS chip.
- AC coupling is compatible with Amp-Sha that adopted the constant current feedback.
- 120e- threshold dispersion without threshold trim reported, very attractive.
- Threshold voltages set by V_{diode} according to $I_{thr} = I_s(e^{V_D/V_T} - 1)$




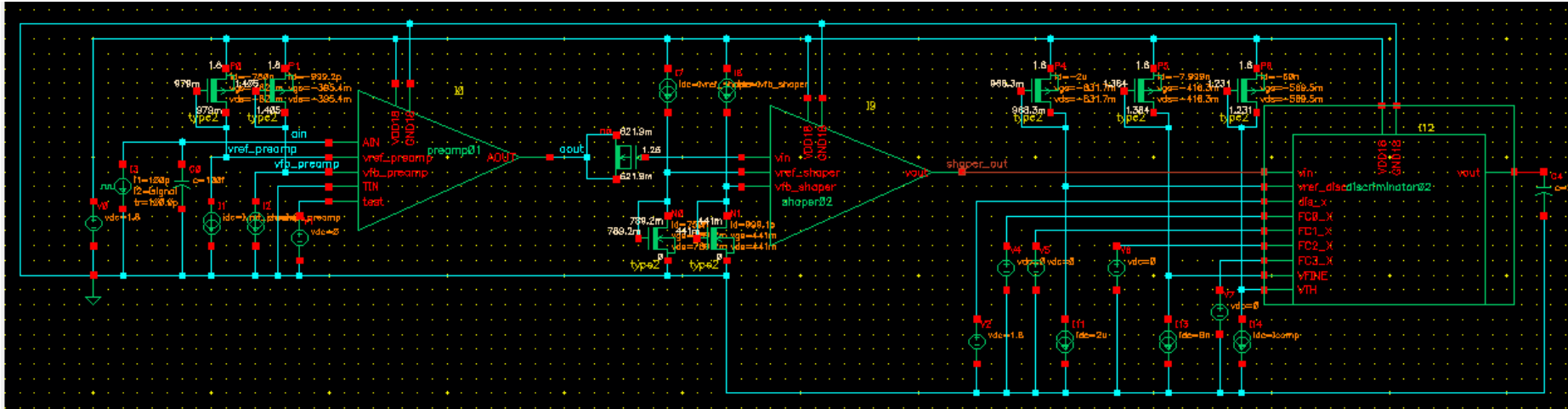Amp-Sha-Disc System designed for CPIXTEG3b




- Constant current feedback Preamp, 5fF feedback capacitor
- AC coupled to shaper, voltage gain of 6
- AC coupled diode-biased inverter discriminator, 4-bit local tuning

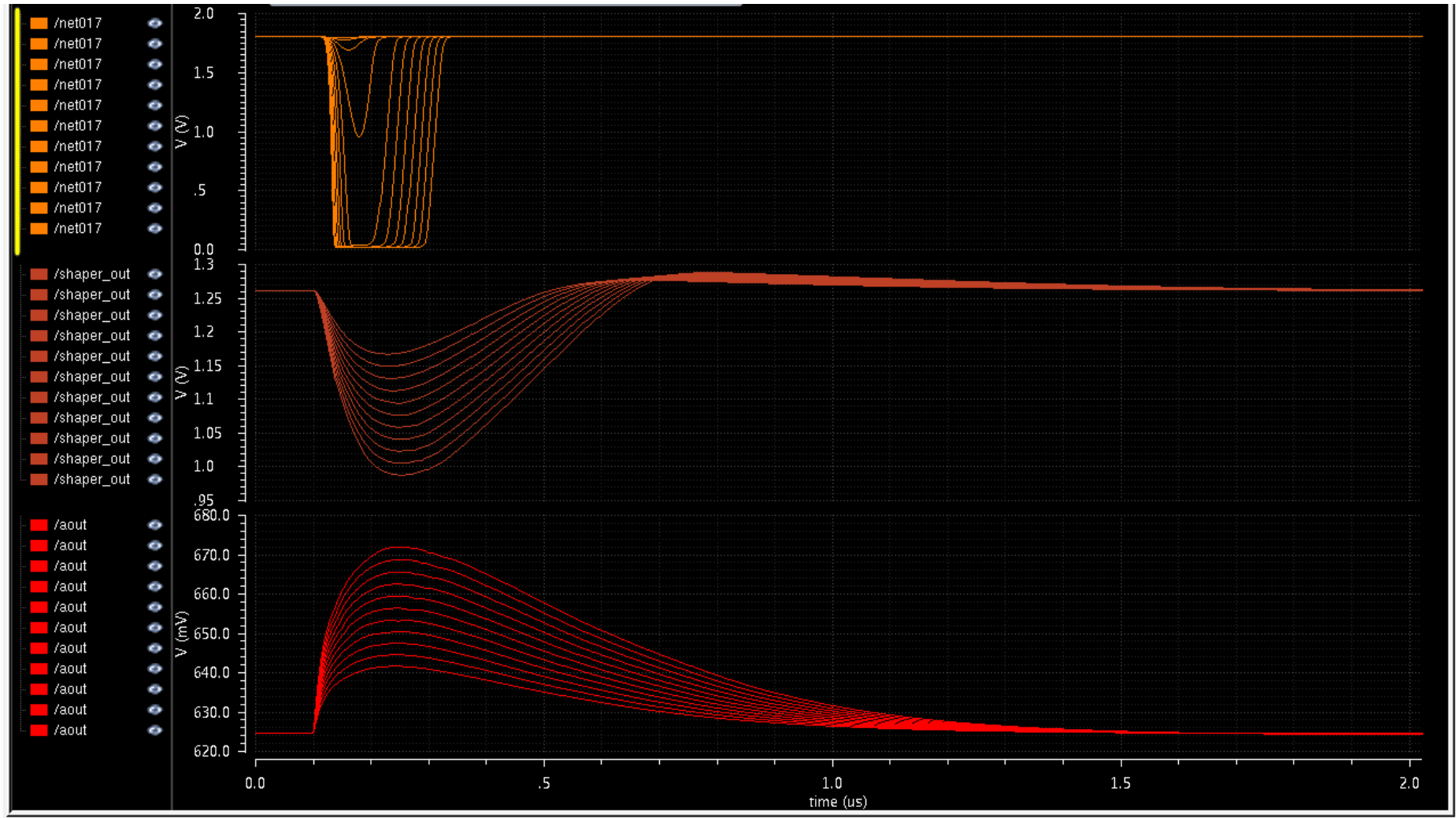$I_{\text{threshold}} (I_0) = 40\text{nA}$, input charge = $750e^-$ to $2000e^-$



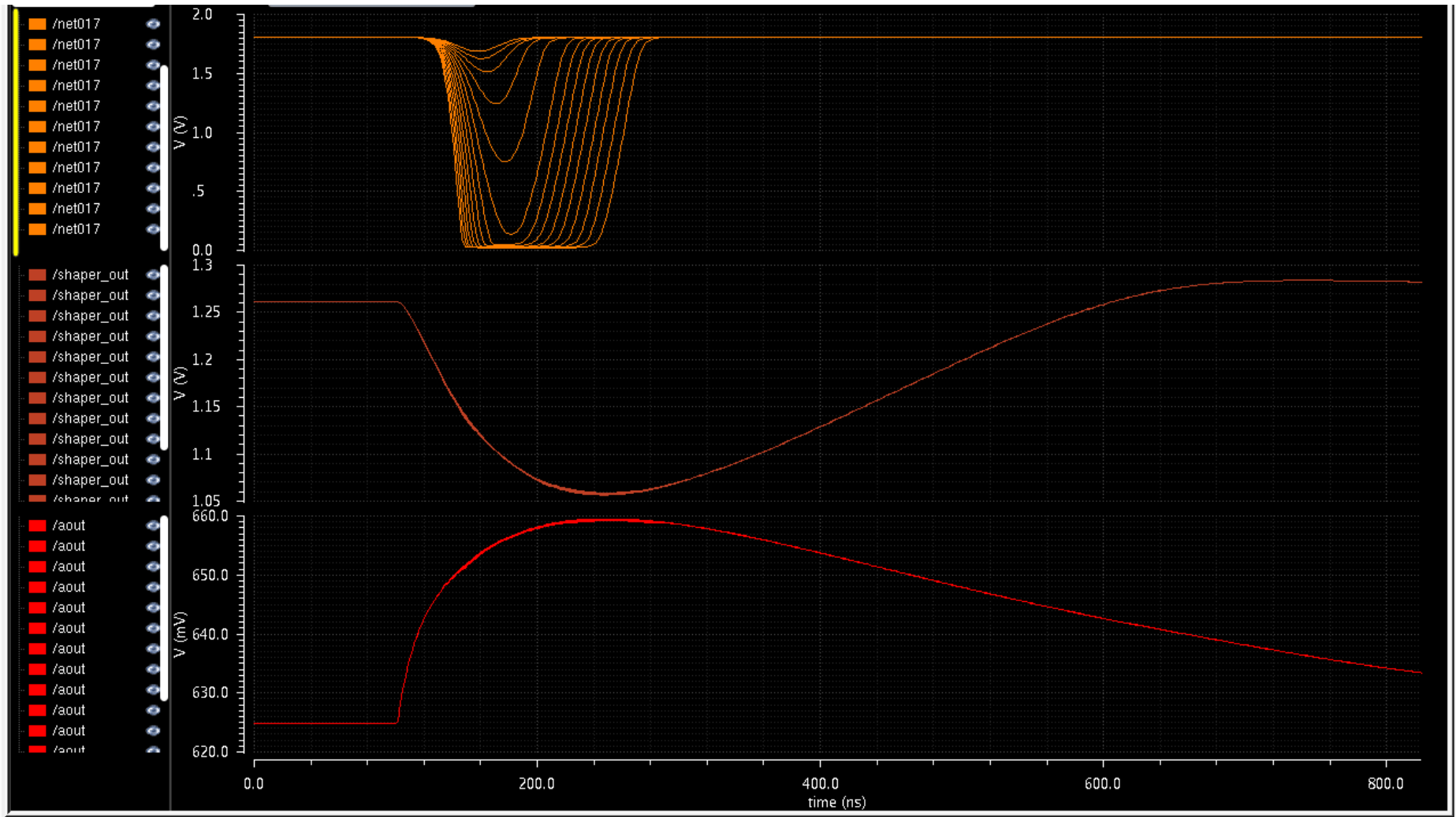
input charge = $1500e^-$, $I_{\text{threshold}} (I_0) = 40\text{nA to } 66\text{nA}$



threshold scan


threshold = 25nA, Assuming $V_{TLH} = 1.3V$ and $V_{THL} = 0.5V$ for the following digital inverter;

Transition btw.
712.5e⁻ and 775e⁻

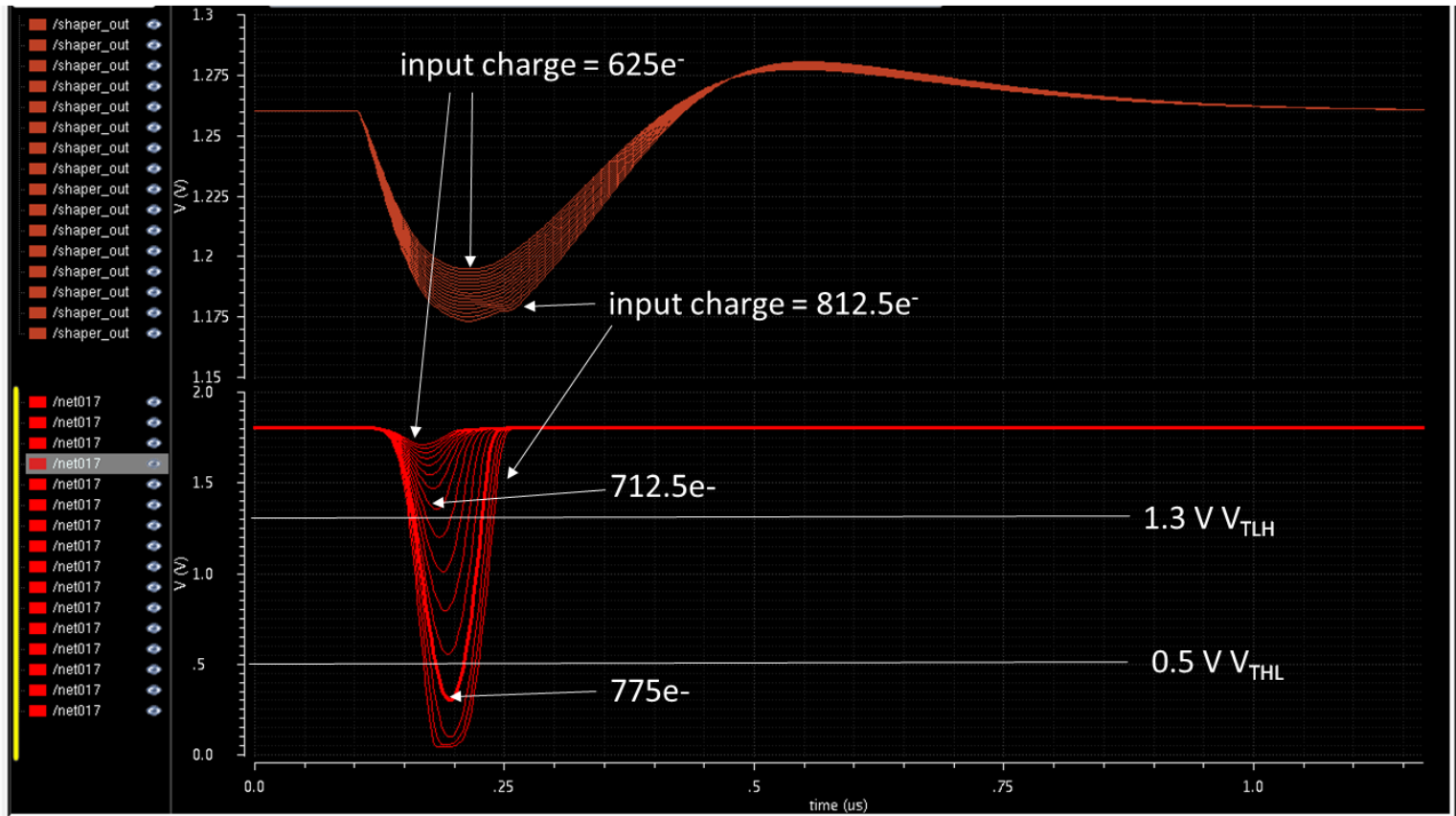

$I_{\text{threshold}}$	input charge (e^-)	Transition charge (e^-)	Average input charge (e^-)
25nA	625-812.5	712.5-775 (62.5)	743.75
75nA	1500-1687.5	1575-1662.5 (87.5)	1618.75
125nA	2375-2562.5	2437.5-2537.5 (100)	2487.5
150nA	2812.5-3000	2875-2975 (100)	2925

Average input charge (e^-)

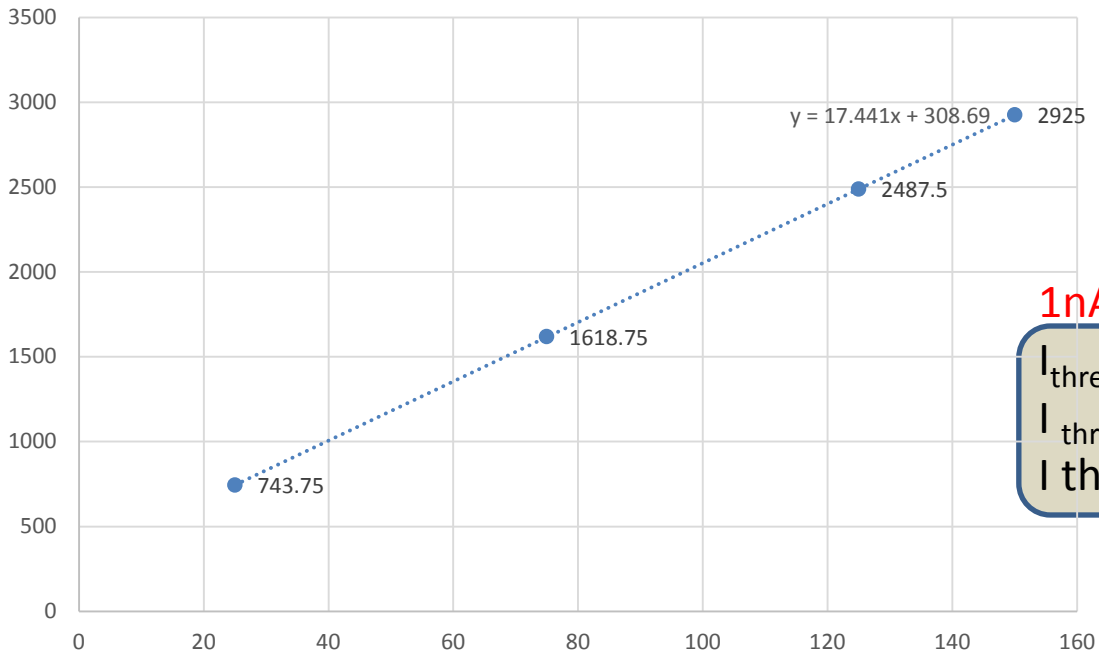

1nA ~ 17.4 e^-

$I_{\text{threshold}}$ Adjustment Range: 25-150nA
 $I_{\text{threshold}}$ tuning step: 2-5nA
 $I_{\text{threshold}}$ tuning DAC: 4 bits or 3 bits

Total Noise Spectrum @ shaper output


Primary noise source: NN1&PP1 of preamp around 2 MHz;

NN1&PP1 of shaper at low frequency;

$SUM = NN1_preamp + PP1_preamp + NN1_shaper + PP1_shaper$

(Total – SUM) is mainly contributed by the Feed-back Tr. (P1) in shaper

V^2/Hz

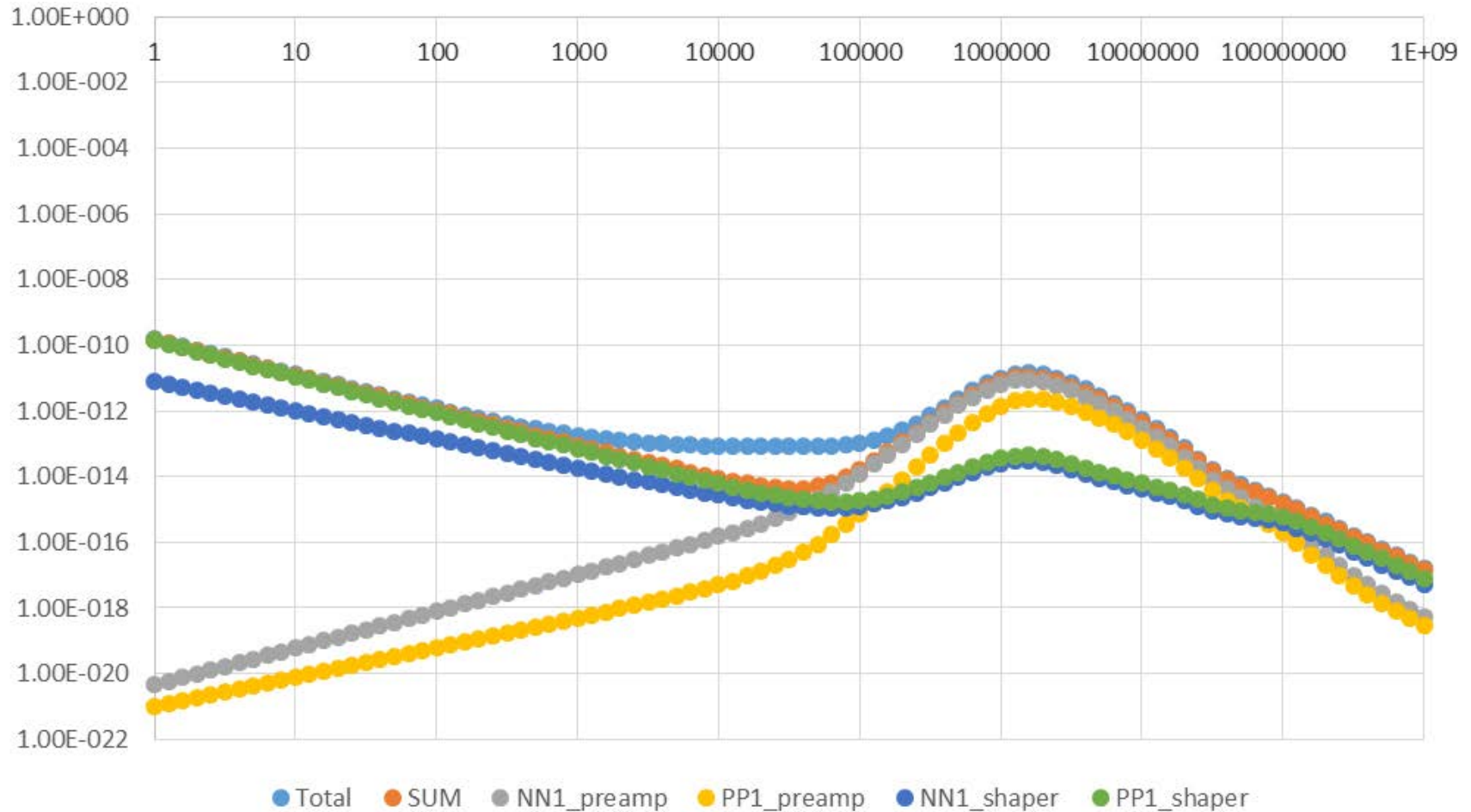

- Noise @ PREAMP Output

- $n_o = 1.4\text{mV}$
- equivalent to $70 e^-$

$C_d = 100\text{fF}$;

$C_f = 5\text{fF}$;

$C_{\text{couple}} = 30\text{fF}$


$I_{\text{fb_preamp}} = I_{\text{fb_shaper}} = 1\text{nA}$;

- Noise @ SHAPER Output

- $n_o = 6.8\text{mV}$
- equivalent to $57 e^-$

ENC (e^-)

ENC @ Shaper Output

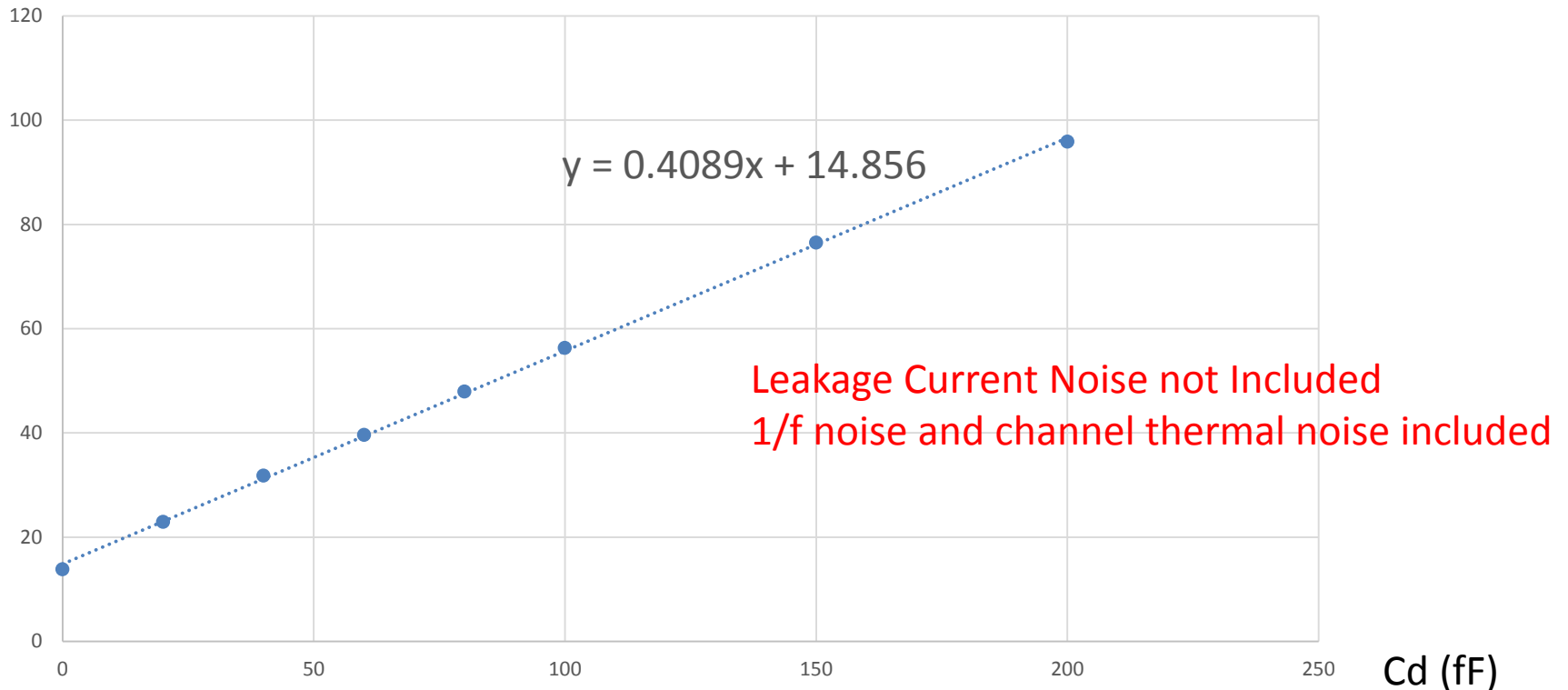


First Test Results of CPIXTEG3b (1)

- Bias current measurement ($V_{IO_BPW} = 0.85V$)
 - Discrepancy between I_{out} and $I_{out_pixel1,2,3}$ affected by V_{IO_BPW} , but required different V_{IO_BPW} to compensate NMOS and PMOS respectively.
 - Error on I_{fb_shaper} not understood.
 - Should be OK to operate the chip on the basis of measurement results.

Current Source	I_{in} (nA)	Current Ratio	I_{out} (nA)	I_{out_pixel1} (nA)	I_{out_pixel2} (nA)	I_{out_pixel3} (nA)
I_{fb_preamp}	-10.5	10:1	-1	-0.49	-0.5	-0.47
I_{fb_shaper}	1.6	10:1	1.4	1.3	1.4	1.4
I_{ref_preamp}	-3000	4:1	-791	-726	-709	-696
I_{ref_shaper}	3000	4:1	1180	1140	1200	1170
I_{thr}	-1500	8:1	-223	-172	-167	-172
$I_{thr_tunning}$	-40	8:1	-4			


First Test Results of CPIXTEG3b (2)

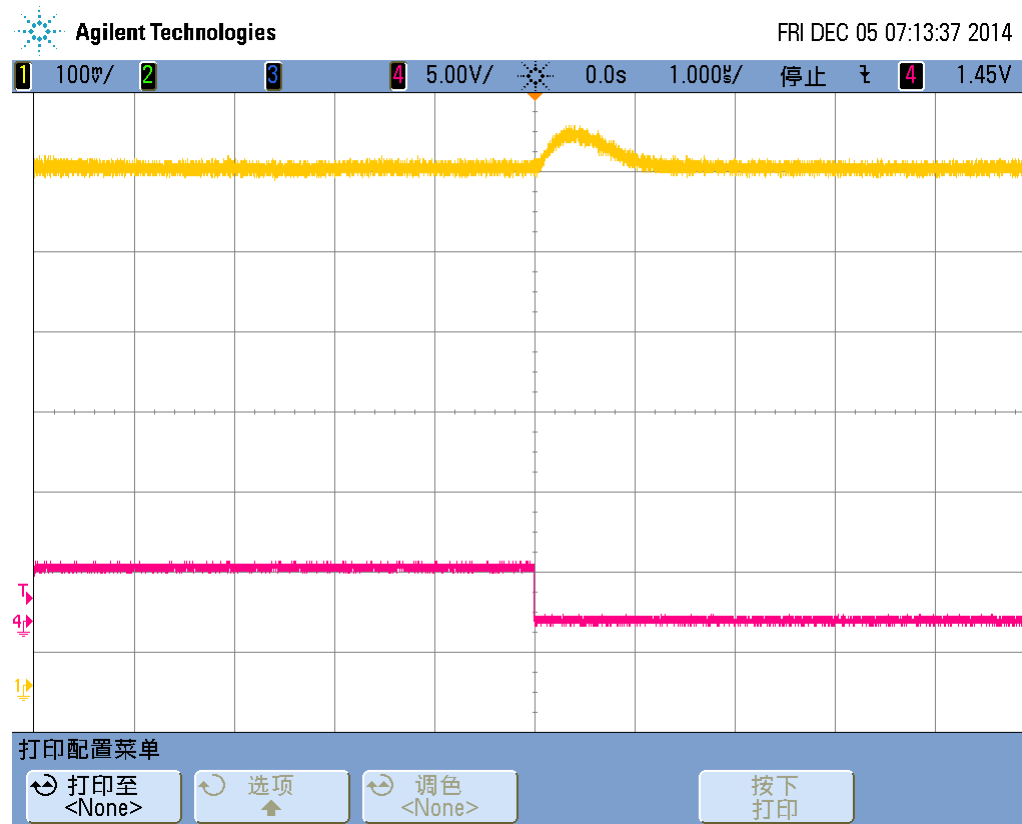- Analog out of Preamp
 - $V_{test} = 80\text{mV}$, equivalent to $1900 e^-$




First Test Results of CPIXTEG3b (3)

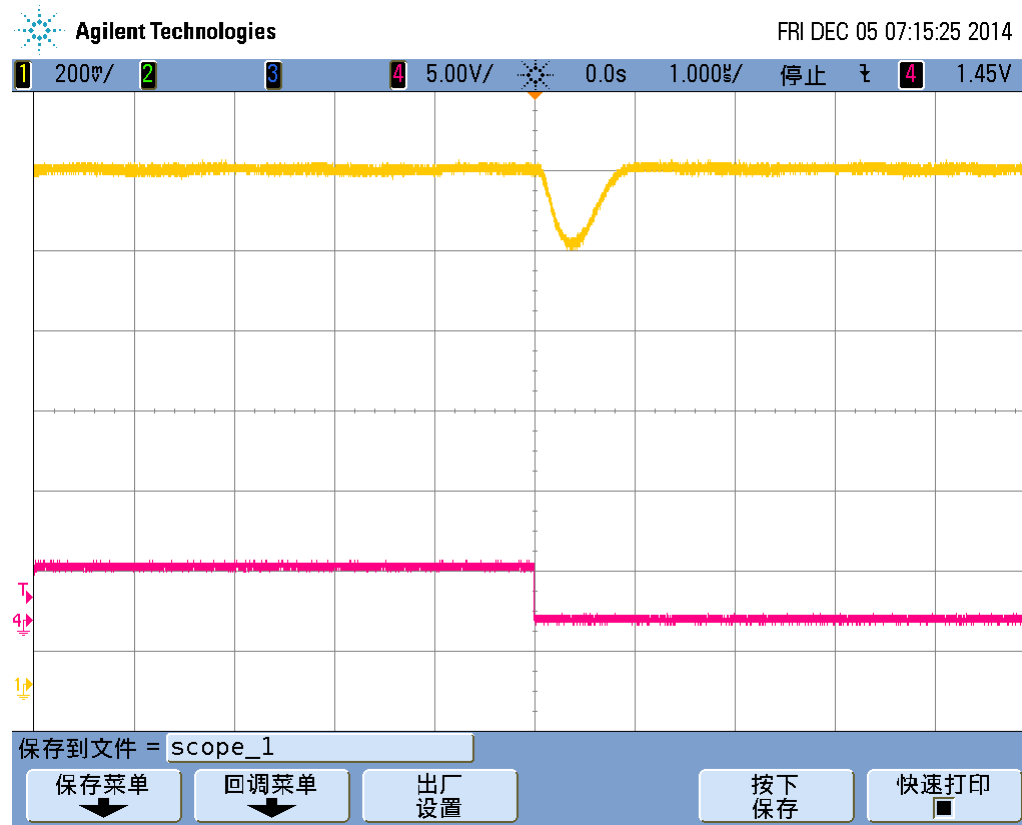- Analog out of Shaper
 - $V_{test} = 80\text{mV}$, equivalent to $1900 e^-$







First Test Results of CPIXTEG3b (4)

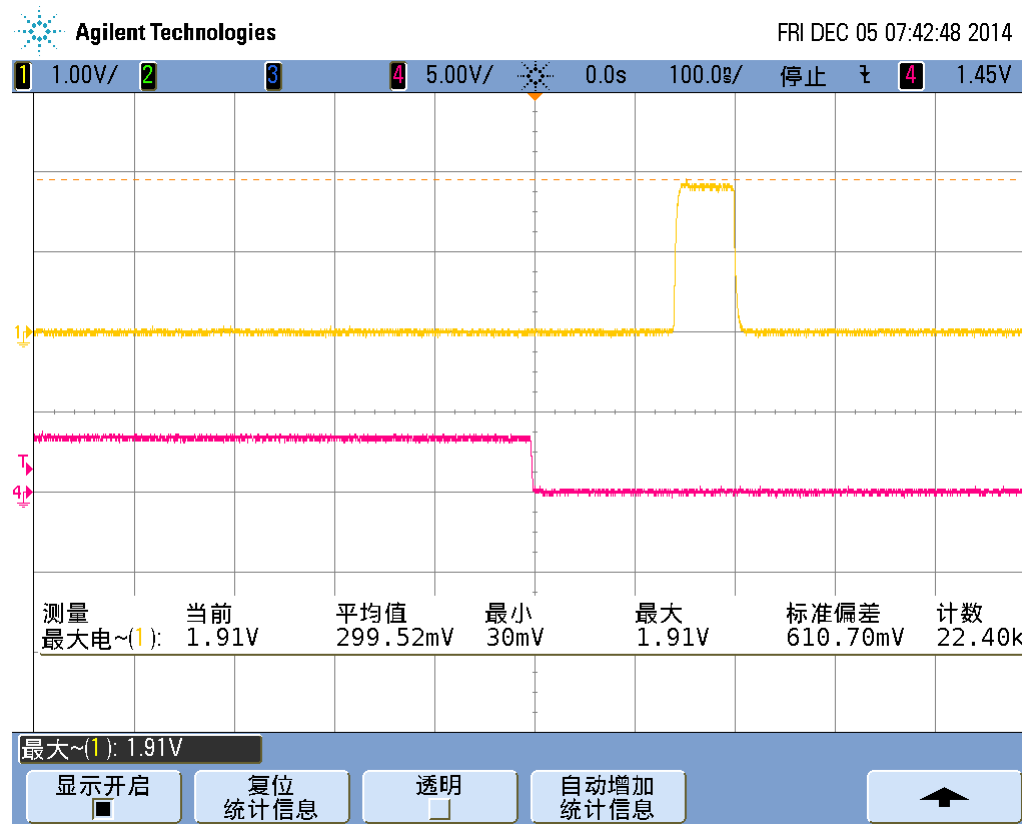- Analog out of Discriminator
 - $V_{test} = 80\text{mV}$, equivalent to $1900 e^-$




First Test Results of CPIXTEG3b (5)

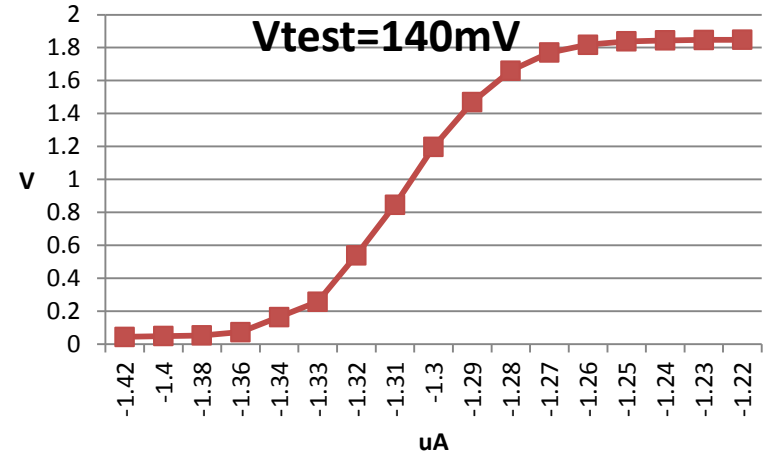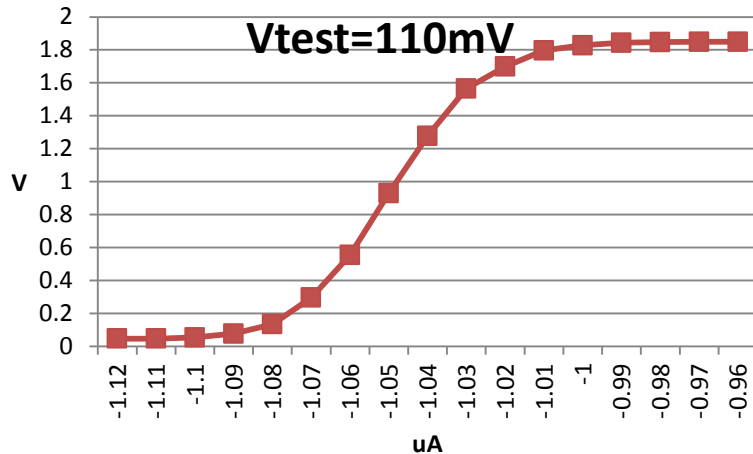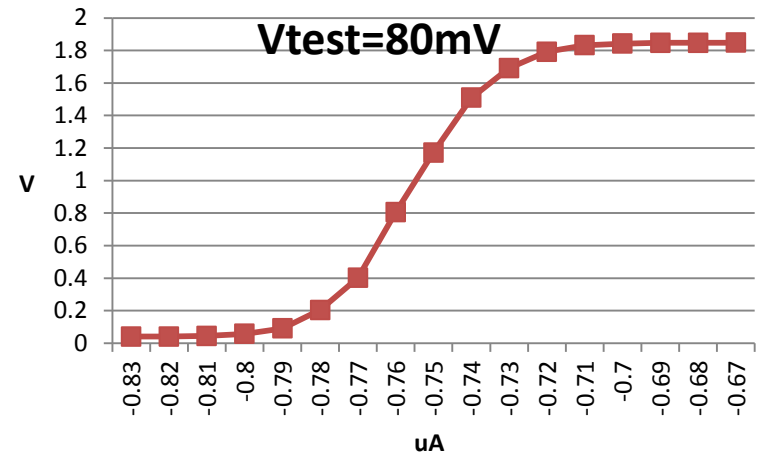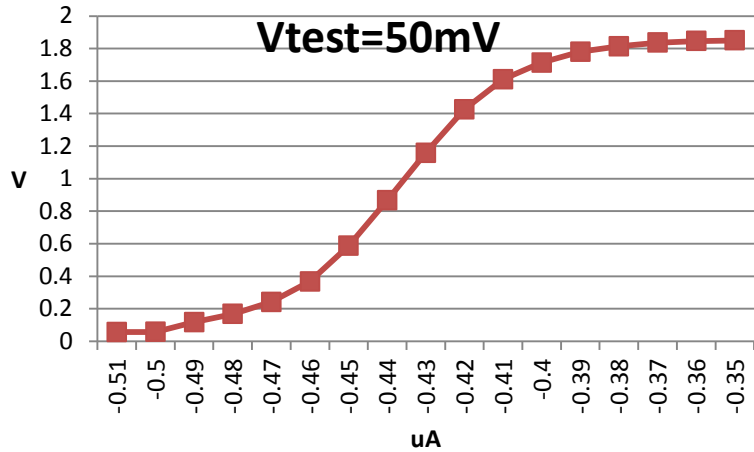- S curve measurement
 - ENC $\sim 27e^-$




Shielding Measurement on CPIXTEG3 (1)

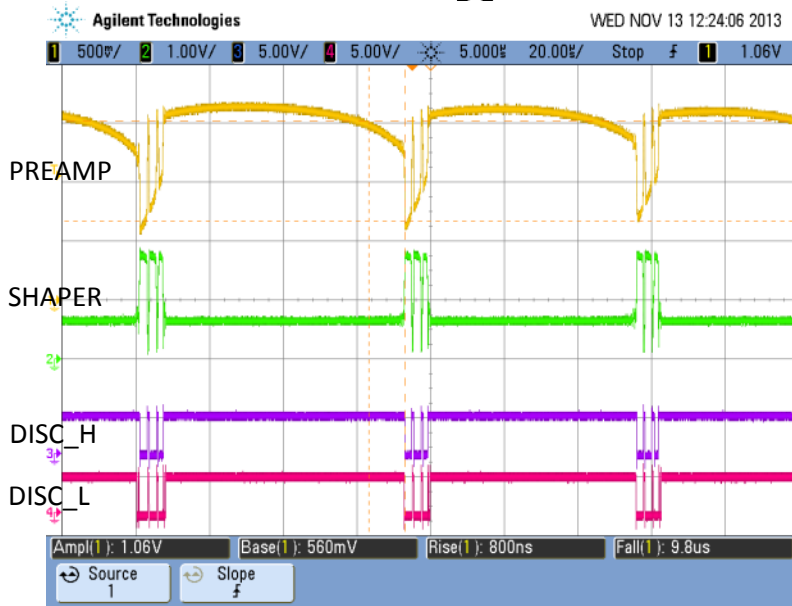


1. Oscillation



Pixel Layout

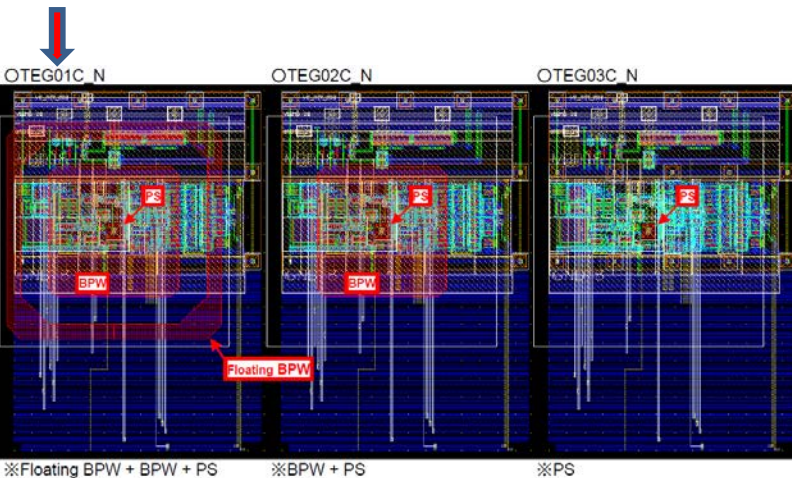

Disable SHAPER
via VH2

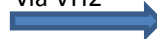

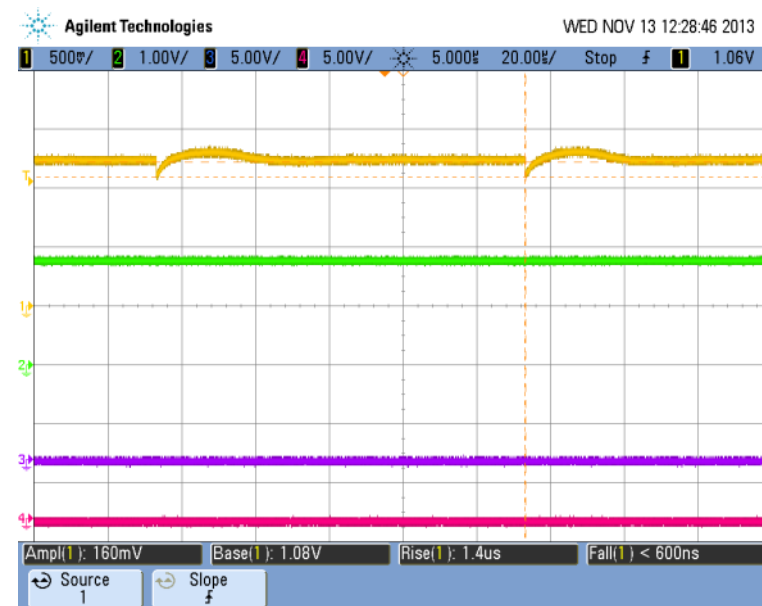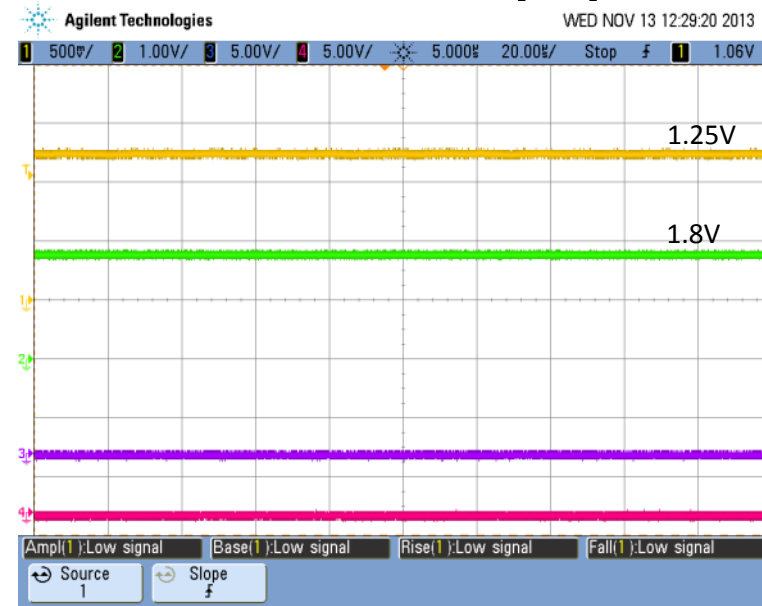2. Oscillation stopped after shaper disabled



$V_{test} = 300\text{mV}$;
 $V_{L_AMP_N} = 300\text{mV}$;
 $V_{det} = +5\text{V}$


3. Response to Charge Injection 300mV

Shielding Measurement on CPIXTEG3 (2)

Vdet = +5V;
 Adjust VL_AMP_N = 0.2V;
 Vtest = 300mV;
 Vthh = 1250mV;
 Vthl = 800mV;
 Glitches can be removed by disabling
 Disc. via DO_EN.




Pixel Layout


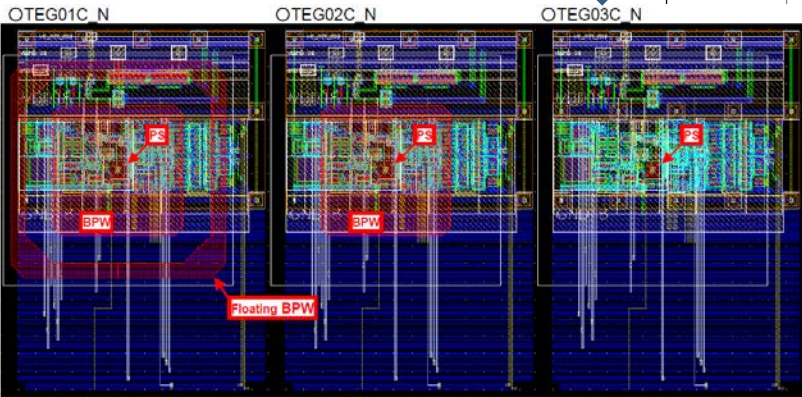


※Floating BPW + BPW + PS ※BPW + PS ※PS


Shielding Measurement on CPIXTEG3 (3)

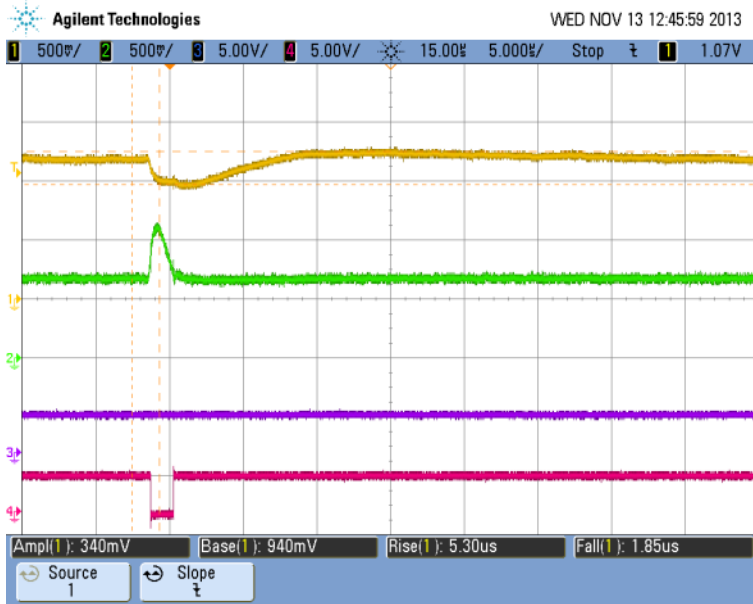

Disable Disc.
via VH2

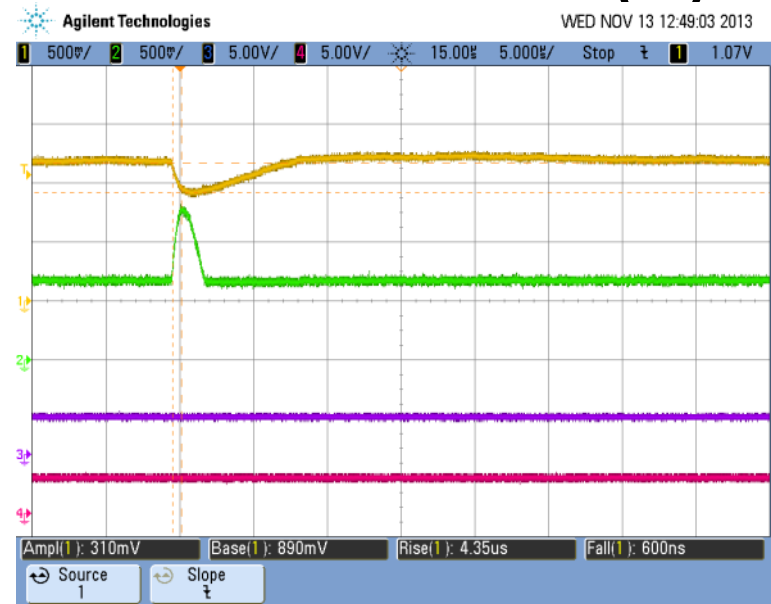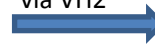

TEG04C_N

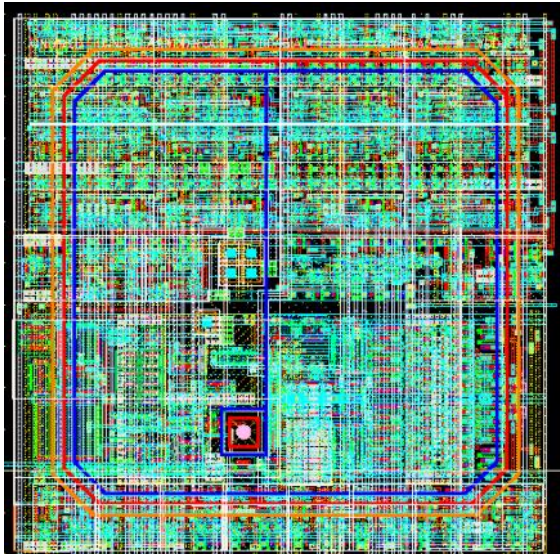


1. Charge Injection with Discr. working

$V_{test} = 600mV$;
 $V_{L_AMP_N} = 280mV$;
 $V_{det} = +5V$

2. Charge injection with Discr. stopped

Shielding Measurement on CPIXTEG3 (4)

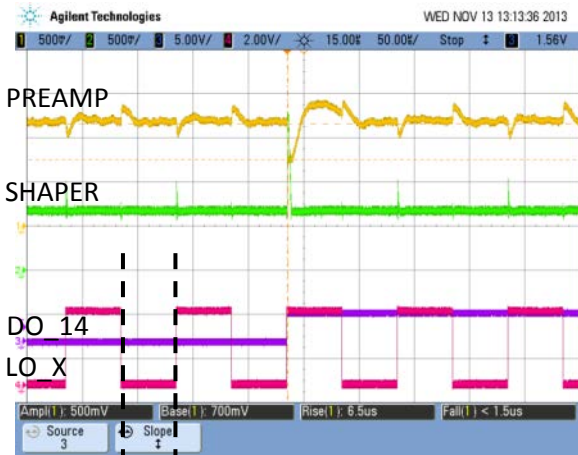


Hit logic operation Counter operation



X011_1111_1111_1111
→X100_0000_0000_0000





X111_1111_1111_1111
→X000_0000_0000_0000

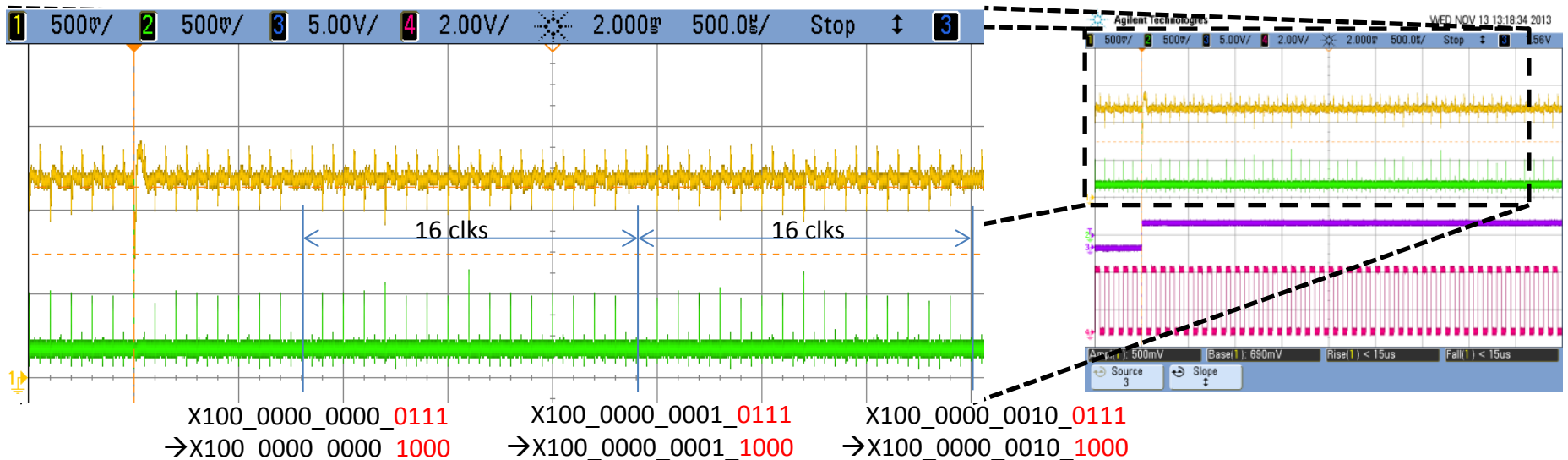

X100_0000_0000_0111 X100_0000_0001_0111 X100_0000_0010_0111
→X100_0000_0000_1000 →X100_0000_0001_1000 →X100_0000_0010_1000

Preliminary results on CPIXTEG3b

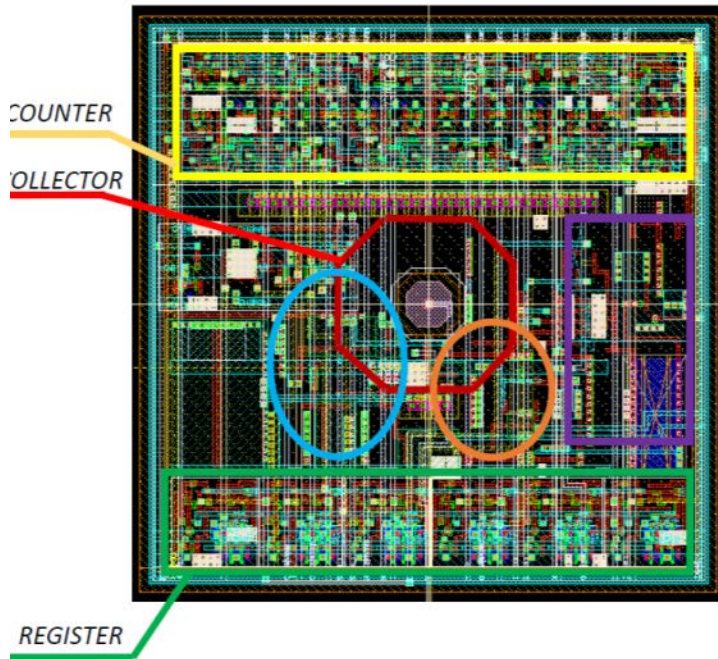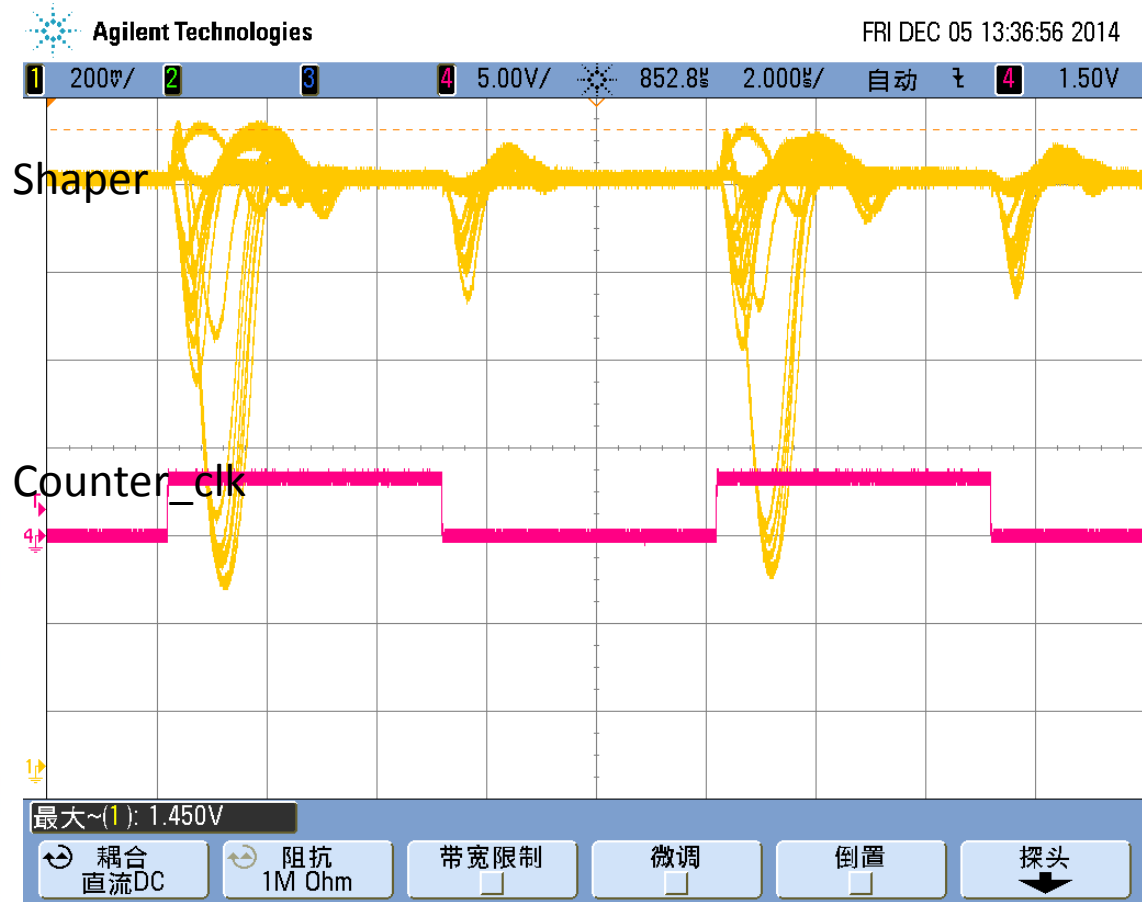First CPIXTEG3b delivered was fabricated on normal SOI wafer. No DSOI at all. Clear crosstalk seen.



Summary

- Shielding is a critical issue in counting pixel chips.
- A new Amp-Sha-Disc system works, which is less dependent on the precision of very low current source.
- Nested-Wells provided shielding between analog and sense node, but no sufficient for shielding digital part in the pixel.
- Small sense node and small pixel is being pursued.